BASIC COMPUTER



At the heart of this versatile and simple to build computer for process control and automation applications is Intel's Type 8O52AH-BASIC microcontroller.

As already noted in reference (1), the Type 8052AH-BASIC VI.1 is a single-chip microcontroller tailored to data manipulation in intelligent instrumentation, measurement and control systems. Not surprisingly, therefore, the 8052AH-BASIC features an extensive and powerful set of input/output and timekeeping functions.

By virtue of its compactness and ease of programming, the BASIC computer described here is suitable for a wide range of domestic as well as industrial applications. Although not every programmer will applaud the use of BASIC, it can be argued that this is still the most widely known, and often first apprehended, programming language. Moreover, the BASIC interpreter of the 8052AH-BASIC is an advanced version offering instructions like DO-WHILE and DO-UNTIL which enable better structuring of programs than the GOTO statement. Also, variables can be stored and retrieved by means of instructions PUSH and POP. The BASIC interpreter is reasonably fast as compared with competetive 8 and 16 bit systems. In conclusion, the 8052AH-BASIC couples the power and versatility of the 8051 to the qualities of a well-written, reasonably fast, BASIC interpreter.

The computer described is suitable for experimental as well as stand-alone applications. Programs can be written, tested, and debugged by anyone with a reasonable command of BASIC. The microcontroller used is not cheap, probably because of its specialist nature, and the fact that it has hitherto found applications mainly in industrial control systems. None the less, the cost of the 8052AH-BASIC is justifiable considering its impressive potential.

To aid programmers in writing efficient programs, Intel sup-

plies the indipensable MCS BASIC-52 USERS MANUAL, which carries reference number 270010-003.

It is important to note that ready-made programs for the BASIC computer are not available. The proposed system is intended primarily for applications where the BASIC programs are not an end in themselves, but where the hardware-software link is readily accessible to enable developing and testing computer controlled systems of a wide variety. Once a program is debugged and known to function satisfactorily, the computer can act as a reliable stand-alone controller.


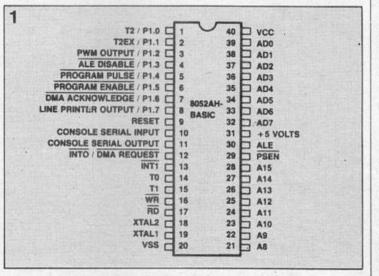


Fig. 1 Pinning of the microcontroller Type 8052AH-BASIC from

Features

The computer described features an on-board EPROM programmer, which is controlled direct by the 8052AH-BASIC CPU. This means that the processor can store its own programs in EPROM after debugging and testing. Once it is EPROM resident, the BASIC program is available for direct

12.26 elektor india december 1987

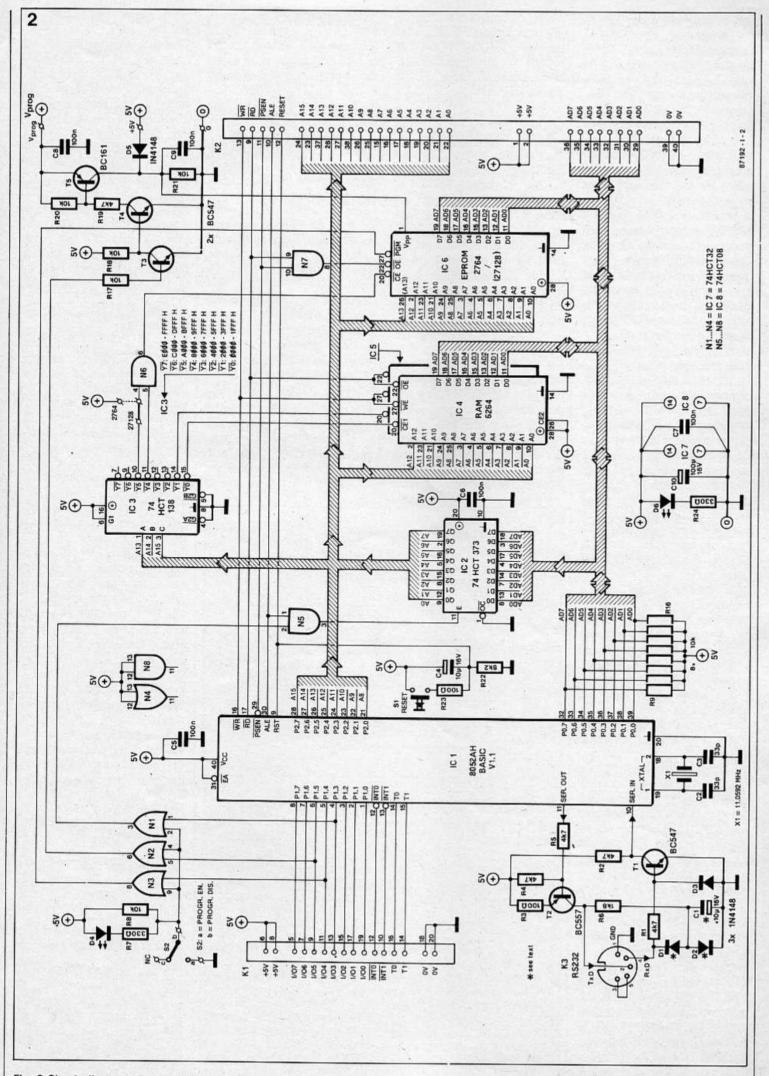

and autonomous execution by the processor. The EPROM contents form the token program listing rather than machine code obtained by a compiling process. The programming of EPROMs on the board is straightforward, and fully supported by BASIC instructions. A single EPROM can hold a number of programs, which can even call each other when necessary.

It should be noted that the

BASIC computer has no keyboard and screen of itself. These communication functions are taken over by an exterconsole (terminal), connected to the computer's bidirectional, serial I/O port. As to the hardware configuration of the proposed BASIC computer, this is characterized by a high degree of flexibility, allowing the user to readily add, say, a UART (universal asynchronous receiver/transmitter), an ACIA (asynchronous communications interface adapter), a number of PIAs (peripheral interface adapter), or other peripheral circuitry such as an alphanumerical display, a sound generator, or a keyboard encoder. The pinning of the 8052AH-BASIC is given in Fig. 1.

The 8052AH-BASIC has a number of powerful timing instructions which, in conjunction with the interrupt statements, special registers, and instruction counters, afford excellent control of time critical I/O applications. A real time clock is also available in the form of function TIME, which offers a resolution of about 5 ms.

The Type 8052AH-BASIC is an 8 bit microcontroller, which means that it combines the functions of central processing unit (CPU), and peripheral circuits (I/O; DMA). The chip has an accumulator A, a register B, a status register PSW (program status word), an 8 bit stack pointer, a 16 or 2x8 bit data pointer DPTR, 4 8 bit ports for use as an I/O and/or address, data, or command bus, a double serial communication register SBUF, 3 register pairs TH0-TL0, TH1-TL1 and TH2-TL2, which together form the 3 16 bit timers T0, T1 and T2, an intermediate storage register pair RCAP2H-RCAP2L for a number of functions of timer 2, and, fivarious command functions: IP (interrupt priority), IE (interrupt enable), TMOD, TCON & T2CON for the timers, SCON (serial control) and PCON (power control).

Circuit description

The circuit diagram of the BASIC computer is given in Fig. 2. The 8 Kbyte BASIC interpreter is internal to the microcontroller, IC1. EPROM IC6 holds the user's BASIC programs. The minimum amount of RAM for the 8052AH-BASIC is 1 Kbyte starting at address 0000. In the present application, the RAM area is either 8 Kbyte (0000-1FFF) or 16 Kbyte (0000-3FFF), depending on whether 1 or 2 RAMs Type 6264 are fitted (IC4: ICs). Write and read operations are controlled direct by signals WR and RD respectively.

The memory structure of the 8052AH-BASIC is not in accordance with von Neumann's model: the program memory is distinct from the data memory,

FFFFh

BFFFh

9FFFh

8000h

3FFF_h

1FFFh

9000

which explains the logic combination of signal PSEN from 8000 to 9FFF; 27128 = ations for the 8052AH-BASIC. efficient dress 8000.

Decoder IC3 divides the memory area in blocks of 8 Kbyte. AND gate Ne makes it possible to combine 2 block select signals when the EPROM used is a Type 27128. Normally, octal latch IC2 demultiplexes the data and lower address bytes with the aid of signal ALE (address latch enable). In the EPROM programming mode, however, the LS address byte is kept latched

(program store enable: control of read operations in an external program memory) with RD in gate N7 to select the ROM memory area (2764 = 8 Kbyte 16 Kbyte from 8000 to BFFF). This does not exhaust all the possible memory configurbut forms a practical as well as combination-see Fig. 3. In the EPROM programming mode, the microcontroller addresses EPROMs in the memory area starting at ad-

> ROM or User I/O (E)EPROM RAM extensions

Fig. 3 Memory structure of the 8052AH-BASIC.

27128

2764

IC 5

IC 4

87192 - 3

Connector K1:		Connector K2:									
Pin	Pin	Pin	Pin	Pin	Pin						
1 NC	2 NC	1 +5 V	11 PSEN	21 A1	31 D2						
3 NC	4 NC	2 +5 V	12 RESET	22 AO	32 D3						
5 1/07	6 +5 V	3 NC	13 WR	23 A14	33 D4						
7 1/06	8 +5 V	4 NC	14 NC	24 A15	34 D5						
9 1/05	10 INT1	5 NC	15 A7	25 A8	35 D6						
11 1/04	12 INTO	6 NC	16 A6	26 A9	36 D7						
13 1/03	14 T1	7 NC	17 A5	27 A11	37 A13						
15 1/02	16 TO	8 NC	18 A4	28 A12	38 A10						
17 1/01	18 1	9 RD	19 A3	29 DO	39 1						
19 1/00	20 1	10 ALE	20 A2	30 D1	40 1						

nally, an array of registers for | Table 1 Pinning of connectors K1 and K2.

much longer than during normal bus cycles.

This also goes for the MS address byte and the datawordthe normal duration of a programming cycle is of the order of 50 ms. The software has no direct control over the length of the ALE pulse, and this is, therefore, inhibited with the aid of N1, Ns and the logic low level on CPU output Pl.3.

When port 0 is used in the I/O mode, pull-up resistors are required on the open drain outputs. Normally, this port functions as the data & address bus, but operates as an I/O port in the EPROM programming mode.

The TTL levels at the serial output, P3.1, of the microcontroller are converted into the corresponding positive and negative levels for the terminal. Rectifier D₁-D₂-C₁ is connected to the terminal's TXD line to provide the negative supply for TXD driver T2. Components D1 and D2 can be omitted, and C1 replaced by a wire link, when the terminal accepts and sends pulses with TTL levels.

The connections on the serial I/O connector, K3, are given in the circuit diagram.

Table 1 shows the pin assignment on connector Ki, which carries the 8 lines of peripheral port Pl, interrupt inputs INTO and INTI, and lines TO and Tl. which form the external inputs of the respective timers. Line pairs WR and RD, RxD and TxD, INTO and INTI, and TO and TI together form port P3 of the 8052AH-BASIC. Apart from their normal use as I/O lines, the lines on port Pl may be used for special purposes. For example, Pl.0 and Pl.1 can provide trigger as well as clock pulses for timer T2. This is a standard function of the 8052, and not a particular feature of the BASIC interpreter. Lines Pl.3, Pl.4 and Pl.5 are used for programming the majority of currently available EPROM and EEPROMs Type 2764 and 27128. Output Pl.6 is connected to input INTO for ready implementation of a DMA (direct memory access) mechanism. Output Pl.7 can act as a direct serial channel for driving, say, a printer, controlled with the aid of commands LIST# and PRINT#. There are more BASIC instructions for port 1: PWM, for example, offers control of the pulsewidth on output Pl.2, while instruction PORTI enables direct read/write access.

The signal assignment on connector K2 is shown in Table 1. This connector carries lines AD0...AD7, A0...Al5, and the command bus, and so enables ready connection of peripheral extension, or DMA, circuitry. It is possible to halt the processor in the idle mode, and so arrange for an external processor or microcontroller to temporarily gain access to the memory in the BASIC computer. The idle mode is initiated with the aid of the corresponding BASIC statement, and can be used for switching the microcontroller to the non-active state when no action on its part is required.

The clock oscillator is internal to the 8052AH-BASIC, and merely requires a quartz crystal and 2 capacitors. The indicated crystal frequency of 11.0592 MHz is required to ensure the correct timing for the serial channel, the real time clock. and the EPROM programming pulses. When it is intended to use, say, a 12 MHz crystal, the processor should be informed this by declaring XTAL=12000000. It should be noted that any oscillator frequency other than 11.0592 MHz may result in reduced accuracy of the counter operations.

The computer is reset and initialized on power up either automatically (R22-C4) or manually (S1). Input EA (external address) is made permanently logic high because the BASIC interpreter is an internal memory area.

Programming EPROMs

The (E)EPROM programming facility of the present BASIC computer is, without doubt, one of its most attractive features. It is important to note that the computer is not just an EPROM programmer, but a data handling and storage system that can be customized as required for the application in question. While communicating with the user via the terminal, the 8052AH-BASIC can edited, debugged and tested BASIC (sub)routines in EPROM to facilitate calling these as "tools" at any time. Before programming is effected, the microsoftware in the 8052AH-BASIC takes care af all the

tokenizing of the object program to ensure compact storage. Depending on the programming mode, certain parameters are stored along with the program, and are instantly available when this is loaded and run. These program parameters include the baud rate, variable MTOP, an autoexecute flag, and a flag that enables skipping the memory initialization routine at poweron-this is particularly useful when the RAM is battery powered.

Finally, it is possible to use BASIC for loading an EPROM with an assembler program that is executed automatically after a RESET pulse.

With reference to the circuit diagram, when line Pl.5 goes low, transistors T₃, T₄ and T₅ ensure that the programming voltage reaches the Vpp terminal of the EPROM. The pro-

Table 2.

Manufacturer	Туре	memory organization	Vpp		
AMD	AM2764 AM2764A AM27128 AM27128A	8K × 8 8K × 8 16K × 8 16K × 8	21 V 12.5 V 21 V 12.5 V 21 V 21 V 21 V		
Fujitsu	MBM2764 MBM27C64 MBM27128	8K × 8 8K × 8 16K × 8			
Hitachi	HN482764 HN27C64 HN482764P HN4827128 HN27128P	8K × 8 8K × 8 8K × 8 16K × 8 16K × 8	21 V 21 V 21 V 21 V 21 V 21 V 12.5 V 12.5 V 12.5 V 12.5 V 12.5 V		
Intel	2764 P2764 2764A 27C64 P2764A 27128 27128A P27128A	8K × 8 8K × 8 8K × 8 8K × 8 8K × 8 16K × 8 16K × 8			
Mitsubishi	M5L2764 M5L27128	8K×8 16K×8	21 V 21 V		
National Semiconductor	NMC27C64 NMC27CP128	8K×8 16K×8	12.5 V 12.5 V		
NEC	µРD2764 µPD27C64 µPD27C64C µPD27C64C µPD27128 µPD27128C	8K × 8 8K × 8 8K × 8 8K × 8 16K × 8 16K × 8	21 V 21 V 21 V 21 V 21 V 21 V		
Rockwell	R87C64 R27C64P	8K × 8 8K × 8	21 V 21 V		
SEEQ	2764 27128	8K×8 16K×8	21 V 21 V		
SGS/ATES	M2764	8K×8	21 V		
Texas Instruments	TMS2564 TMS2764 TMS27128	8K×8 8K×8 16K×8	25 V 21 V 21 V		
Thomson- CSF	ET2764	8K×8	21 V		
Toshiba	TMM2764 TMM2764DI TMM27128	8K×8 8K×8 16K×8	21 V 21 V 21 V		

The type indications as given may be followed by an access time specification.

Table 2 Programming voltages for a number of EPROM types that can be loaded by the BASIC computer.

gramming voltages for a number of EPROMs are listed in Table 2. The microcontroller places the LS address byte onto lines AD0...AD7, disables ALE by making Pl.3 logic low. The address byte remains latched in IC2 during the remainder of the programming cycle. The MS address byte is placed onto lines A8...A15, and the databyte onto lines D0...D7 of the EPROM to be programmed. Then, output Pl.4 is made logic low, and the byte is programmed in the EPROM because PGM goes low while Vpp is applied. Instructions PROG and FPROG select a duration of the programming cycle of 50 and 1 ms, respectively. FPROG uses the intelligent programming algorithm, and may require raising the EPROM supply voltage from 5 to 6 V. which is not supported by the proposed circuit. Details on the intelligent programming algorithm can be found in reference (2). In all cases, the duration of the PGM pulse is determined by the clock frequency of the microcontroller, and operator XTAL should be defined as as discussed previously. Switch S2 enables blocking the 3 programming signals. This is done for reasons of security because port Pl can be used for purposes other than programming EPROMs.

Up to 255 BASIC modules can be held in a single EPROM, and each of these can call any of the others. The 8052AH-BASIC automatically assigns a number to each BASIC program before storing this in EPROM. The number is sent to the terminal for the programmer's reference. Loading and running a particular BASIC module is effected with the aid of commands ROM X followed by RUN. Variable X is the number of the relevant module. Modules can be copied from EPROM to RAM by means of command XFER.

The programmer has direct access to an extensive library of routines in the BASIC interpreter. Also, BASIC allows calling external machine code subroutines provided by the user. It should be noted, though, that writing (fast) machine code requires an 8051 assembler, and, of course, considerable experience in working at the assembly code level.

The practical use and operation of the EPROM programming facility is extremely straightforward. All that is required is to fit an EPROM in the socket for IC6, apply the correct programming voltage, switch S2 to PROG. EN, load the BASIC file in RAM, and issue command PROG. The other programming commands.

(F)PROG1...(F)PROG6 enable storing auxiliary program information, including the baud rate indicator, and the autoexecute flag. The available options are described in the previously mentioned programming manual from Intel.

Construction

It should be reiterated that the computer described is intended mainly as an aid in developing software and hardware for automated processes and stand-alone, intelligent, controllers or data loggers, where timekeeping is an essential requirement.

The printed circuit board for the BASIC computer is doublesided and through-plated. The component mounting plan is given in Fig. 4.

It is recommended to fit good quality sockets for all ICs. The socket for EPROM IC6 can be a type with turned pins, although a ZIF (zero insertion force) socket mounted as shown in the photograph of the prototype is probably the best solution. Be sure to purchase a microcontroller Type 8052AH-BASIC V1.1. Connectors K1 and K2 are intended for extensions, and need not be fitted as yet. Initially, a single RAM, IC4, is sufficient, since it offers a memory area of about 7 Kbyte for BASIC programs. Resistors R9...R16 2764 and a 27128.

EPROM IC6 is not required to make the circuit function. It is not fitted until it can be pro-

incl. form an 8-way SIL network, but it is also possible to use 8 ordinary resistors, mounted vertically and commoned by a short length of wire connected to +5 V as shown in Fig. 5. The function of the LEDs, D4 and D6, is evident from the circuit diagram. The supply and programming voltage are applied to the circuit via soldering pins and mating sockets, insulated with the aid of heat shrink sleeving. Do not confuse the Vcc and Vpp connections. The PROG. EN switch, S2, and the EPROM selector, S3, may each be replaced by 3 pins and a mating jumper if it is not intended to frequently program EPROMs, or change between a

Semiconductors:

Parts list

Resistors (±5%):

R3;R23 = 100R

R7;R24 = 330R

R6 = 1K8

R22 = 8K2

Capacitors:

C1;C4=10µ; 16 V

C10 = 100µ; 16 V

C2;C3 = 33p ceramic

C5...C9 incl. = 100n

R1;R2;R4;R5;R19 = 4K7

R8;R17;R18;R20;R21 = 10K

R9. . . R16 = 8-way 10K SIL

network, or 8 10K resistors

D1;D2;D3;D5 = 1N4148 D4 = green LED De = red LED T1;T3;T4 = BC547 T2 = BC557 T5 = BC161

IC1 = 8052AH-BASIC VERSION 1.1'

IC2 = 74HCT373 IC3 = 74HCT138 IC4;IC5 = 6264 8Kx8 static **CMOS RAM** IC6 = 2764 or 27128 (see text) IC7 = 74HCT32 IC8 = 74HCT08

Miscellaneous:

S1 = Digitast SPST push button. S2 = miniature SPST switch. K1 = 20-way right angled IDC header with side latches. K2 = 40-way right angled IDC header with side latches. K3 = 5-way DIN socket for PCB edge mounting. X1 = 11.0592 or 11.059 MHz, HC18 enclosure. 28-way ZIF socket. Jumpers and soldering pins as required. PCB Type 87192 (available through the Readers Services). Suitable ABS or metal enclosure. Suitable power supply.

It is regretted that a ready-made front panel for this project is not available.

Intel distrubutors are listed on InfoCard 505 in the March 1987 issue of Elektor Electronics.

The chip is also available from Universal Semiconductor Devices Limited • 17 Granville Court . Granville Road . Hornsey . London N4 4EP. Telephone: (01 384) 9420. Telex: 25157 usdco g. Fax: 01 348 9425.

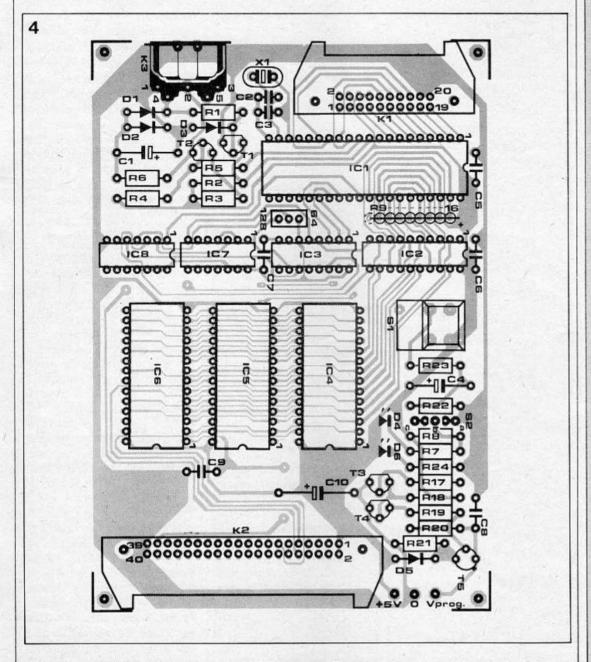


Fig. 4 Component mounting plan for the BASIC computer. The circuit board is available ready-made through the Readers Services.

Fig. 8 SENDBAS.COM has completed sending a program to the BASIC computer via the COM1: port on a PC turbo XT. The baud rate is 1200.

Fig. 9 The BASIC computer is on line again, and has received a program for controlling a polarmount satellite dish position system. Note the system's welcome message at the top of the screen, and the status line of PROCOMM® at the bottom.

Table 5.

SENDBAS.COM was tested in conjunction with PROCOMM® 2.4.2, a versatile communication program for PCs and compatibles. BASIC text files were prepared and stored onto disk in DOS text format using the wordprocessor WORDPERFECT 4.2. Other combinations of communication program and wordprocessor should also work, as long a the files for sending to the BASIC computer are written in DOS text (ASCII) format, i.e., without all the control codes specific to the wordprocessor used. As to the communication program, it is very practical if this offers a SHELL or DOS Gateway command to temporarily switch to DOS, start SEND-BAS for loading the updated file, and return to the BASIC computer by means of EXIT. SENDBAS takes over the set baud rate, and awaits the > prompt from the computer before it sends a new line via COMI: The writing of the file can be seen on the screen. After sending a file using SENDBAS, and EXITing DOS to return to the comms program, type a <CR> when the BASIC computer displays

READY

Type LIST to check the contents of the new program, and run it... The use of SENDBASCOM on a PC-XT turbo is illustrated in Figs. 8 and 9.

A simple filehandler for the BBC micro is listed in Table 5. This program works in conjunction with the well-known wordprocessor VIEW, the micro's serial outlet and the communi-COMprogram cation MUNICATOR, set up for VT52 emulation, XON/OFF, and, say, 9600 baud I/O. It is assumed here that the user is thoroughly familiar with these programs, and the way they are called up and exited. Test the communication between the BBC micro and the BASIC computer by pressing RESET and then the space bar as outlined above. Owners of a MASTER micro can avail themselves of the built-in terminal, obviating the need to purchase a separate communication program.

Leave COMMUNICATOR, run BASIC, and enter the listing of Table 5. Run the program. It creates a small machine code routine called PRDR-52 (printer driver for 8052AH-BASIC), which is automatically saved onto disk. Select the computer's serial output channel by typing FX5,2. Call up VIEW (*W), and load or write the program (i.e. text file) for the BASIC Install computer. PRDR-52 on the serial port by typing PRINTER PRDR-52 at the command level. The VIEW file is now sent to the BASIC computer at the specified baud rate. The fact that VIEW can not send but complete pages is of no consequence. Leave VIEW and run the terminal emulation program to control the BASIC computer direct.

```
LIST
 18 MODE 7
 20 FOR ADDRESS=&4200 TO &426B
38
   READ BYTE
     ?ADDRESS=BYTE
40
50 NEXT ADDRESS
60
   XSAVE PRDR-52 4200 4300 0400 0400
 70 END
80 DATA &4C.&40,&04.&4C.&0F.&04.&4C.&26.&04.&4C.&3C.&04.&4C.&3D.&04
90 DATA &48,&8A.&48,&93,&48,&A9,&02,&20,&EE.&FF,&A9,&02,&A2,&01.&20
100 DATA &F4.&FF.&68.&A8.&68.&AA.&68.&6.&48.&8A.&48.&98.&48.&A9.&83
110 DATA &20.&EE.&FF.&A9.&02.&A2.&00.&20.&F4.&FF.&68.&A8.&68.&AA.&68
120 DATA &60.%A0.%A0.%60.%SD.%FE.%04.%48.%SA.%48.%98.%48.%AD.%FE.%04
130 DATA &C9,&0D.&F0,&09,&20,&EE,&FF,&68,&A8,&68,&AA,&68,&60,&20,&E7
148 DATA &FF.&28.&E0.&FF.&C9.&0A.&D0.&F9.&20.&E0.&FF.&C9.&3E.&D0.&F2
150 DATA &4C.&52.&04
                                                        87192-T5
```

Table 5 This program creates PRDR-52, the filehandler for the BBC micro running VIEW and COMMUNICATOR.

References:

- (1) Single-chip microcontrollers. Elektor India, October 1987.
- (2) MSX extensions 5: EPROM programmer (2). Elektor India, May 1987.

Procomm® is a registered trademark of Datastorm
Technologies, Inc. • PO Box 1471 • Columbia MO 62205 • USA. BBS: (314) 449-9401 (24 h.).

MCS-51® is a registered trademark of Intel Corporation.

handshaking procedure is shown in Fig. 7.

Table 4 is a hex dump of a simple filehandler for IBM PCs and compatibles. The program is called SENDBASCOM, and was written by H Peters. It loads (ASCII) BASIC files from disk, and sends these to the BASIC computer via serial port COMI:, in accordance with the previously mentioned prompt-based handshaking arrangement.

The program is loaded and written onto disk with the aid of DEBUG, which can be found on the DOS disk (use version 3.1 or later). Format a new disk, and copy DEBUGCOM onto it. Select the relevant drive, e.g. B:. Follow this instruction if you are unfamiliar with the operation of DEBUG:

DEBUG<CR>

Fill a 256 byte block with nulls:

F 0100 01FF 00<CR>

Name the program:

NSENDBAS.COM < CR >

Ready for entering the 256 bytes:

E 100 < CR >

Enter the bytes (not the addresses) in Table 4, starting with B4. The first 2-byte address on each line is irrelevant in this case. Use the hyphen for corrections, and the space bar to proceed to the next byte. Type <CR> when the block is complete, and check the screen against the data in Table 4. If necessary, consult the chapter on DEBUG in your DOS manual.

Call up the block pointers:

RCX < CR >

and type

00FF < CR >

after the colon. Do the same with

RBX < CR >

and again

OOFF < CR >

Write the COM file to disk:

Table 3.

COMMANDS	STATEMENTS		OPERATORS				
RUN CONT LIST LIST# (V1.1) NEW NULL RAM ROM XFER PROG1 PROG2 PROG3 (V1.1) PROG6 (V1.1) PROG6 (V1.1) PROG6 (V1.1) FPROG1 FPROG2 FPROG3 (V1.1) FPROG6 (V1.1) FPROG6 (V1.1) FPROG6 (V1.1) FPROG6 (V1.1) FPROG6 (V1.1) FPROG6 (V1.1)	BAUD CALL CLEAR CLEAR(SAI) CLOCK(TAO) DATA READ RESTORE DIM DO-WHILE DO-WHILE DO-WHILE ND FOR-TO-STEP NEXT GOSUB RETURN GOTO ON-GOTO ON-GOTO ON-GOSUB IF-THEN-ELSE INPUT LET ONERR ONER	ONTIME PRINT # PRINT# PRINT@ (V1.1) PHO.# PHO.@ (V1.1) PH1.# PH1.# (V1.1) PGM (V1.1) PUSH POP PWM RETI STOP STRING UI(1&0) U0(1&0) LD@ (V1.1) ST@ (V1.1) IDLE (V1.1) BROM (V1.1)	ADD (+) DIVIDE (/) EXPONENTIATION (**) MULTIPLY (*) SUBTRACT (-) LOGICAL AND (AND.) LOGICAL AND (AND.) LOGICAL AND (OR.) LOGICAL NOT (OR.) ABS() INT() SGN() RND LOG() EXP() SIN() COS() TAN() ATN() -> -< -< ASC() CHR() CBY()	DBY() XBY() GET GET IE IP PORT1 PCON TCON TCON TIMER TIMER TIMER XTAL MTOP LEN FREE PI			


Table 3 Overview of the instructions supported by the 8052AH-BASIC.

W<CR>

Leave DEBUG:

Q<CR>

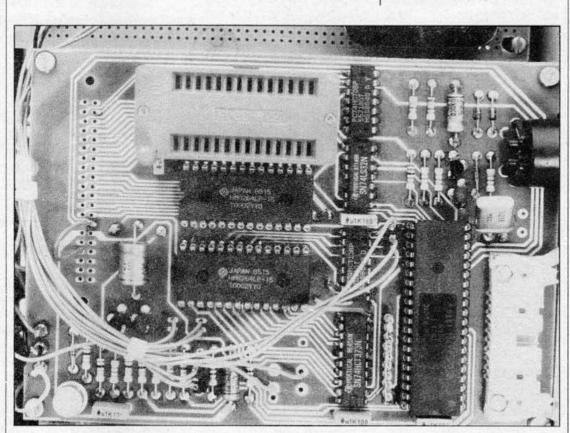The PC filehandler is now available on disk, and can be called with command SENDBAS. Test the program: the screen is cleared, and the text ENTER FILENAME: is displayed. Type <CR> to return to the DOS command prompt.



A close look at the component side of the populated board (prototype version)

	NDB	45.0	COM													
-D 0100 01	FF															
1E48:0100	B4	00	BØ	02	CD	10	8C	C8-05	10	00	8E	DB	BB	ED	00	
1E48:0110	53	E8	38	00	7A	26	E9	94-00	5B	84	07	43	53	3C	1A	S.;.z&[CSc
1E48:0120	74	F4	3C	ØA.	74	16	B4	01-BA	00	00	CD	14	B4	02	BA	t. (.t
1E48:0130	00	00	CD	14	B4	02	8A	DØ-CD	21	EB	DD	B4	02	BA	00	
1E48:0140	00	CD	14	8A	DØ	B4	02	CD-21	3C	3E	75	EF	EB	CA	B4	! Ou
1E48:0150	09	BA	BØ	00	CD	21	B4	ØA-BA	CB	00	CD	21	BB	CC	00	
1E48:0160	8A	07	3C	00	75	03	EB	45-90	BB	CD	00	B9	1E	00	8A	
1E48:0170	07	3C	ØD	74	06	43	E2	F7-EB	05	90	BØ	00	88	07	B4	. (.t.C
1E48:0180	3D	BA	CD	00	BØ	00	CD	21-8B	DB	B4	3F	B9	FF	FF	BA	. =
1E48:0190	ED	00	CD	21	88	DB	B4	3E-CD	21	BØ	20	B4	01	BA	00	
1E48:01A0	00	CD	14	BØ	ØD	B4	01	BA-00	00	CD	14	C3	5B	CD	20	
1E48:01B0	ØD.	ØA.	ØA	ØA	ØA	20	20	20-20	20	45	4E	54	45	52	20	ENTER
1E48:01C0	46	49	4C	45	4E	41	4D	45-3A	20	24	1E	00	00	00	00	FILENAME: \$
1E48:01D0	00	00	00	00	00	00	00	00-00	00	00	00	00	00	00	00	
1E48:01E0	00	00	00	00	00	00	00	00-00	00	00	00	00	14	26	00	
1E48:01F0	74	09	E8	40	E1	E8	1B	F1-E8	BC	E1	A1	D6	26	A3	04	t@

Table 4 Hexdump of SENDBAS.COM, the filehandler for PCs and compatibles.

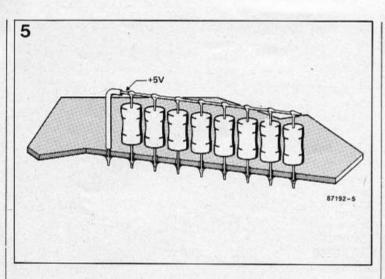


Fig. 5 Showing the use of 8 ordinary resistors instead of a SIL network.

grammed with BASIC modules, and only when the computer is turned off.

The power supply for the BASIC computer can be a simple type with regulated outputs for 5 V (500, mA), and the programming voltage(s).

Initially, the CPU and the memory chips are not fitted while the completed board is fed with Vcc and Vpp. Consult the circuit diagram and carefully check the presence of the supply voltage at all the relevant points. Make sure that there is no short circuit around pin 28 of ICs, since the programming voltage is carried nearby. Switch off the power, carefully fit the CPU and the RAM(s) with the correct orientation, and switch the power on again.

Communication: the terminal

The serial data format for the BASIC computer is:

8 data bits, no parity, 1 stop bit.

Most terminals, consoles, or terminal emulation programs for computers can support this format.

The 3-wire connection between the BASIC computer and the terminal is shown in Fig. 6. At the terminal side, it may be necessary to hard wire a number of RS232 hanshaking lines—consult the relevant documentation. A solution that works in most cases is to connect the following pins in the 25-way RS232 connector:

4-5-8 and

6-20 (sometimes 6-20-22). Where - denotes the connection. The BASIC computer has an internal baud rate timing routine. Press RESET, wait a second or so, and press the space bar on the terminal. The message

*MCS-51(tm) BASIC VI.1 READY

is displayed on the terminal screen, and the BASIC computer is ready to accept commands.


After RESET is pressed, the CPU initializes its internal RAM, and a number of pointers and registers. It then tests, initializes, and determines the size of the external memory area (IC4 and ICs). Next, the memory size is stored with the aid of operator MTOP (memory top), operator XTAL is defined (default: 11059200), and, finally, the CPU reads the data at address 8000 to check for a valid baud rate definition, programmed in EPROM ICs. When a baud rate byte is found, it is stored in register T2CON. The computer then skips its automatic baud rate timing routine and operates at the preprogrammed serial speed, obviating the need for the terminal operator to press the space bar after actuating RESET on the BASIC computer.

The maximum baud rate is 38.4 Kbit/s, and timing characters other than 20H (space) are not accepted.

To verify the correct operation of the system, type

PRINT XTAL,TMOD,TCON, T2CON <CR>

to which the computer replies

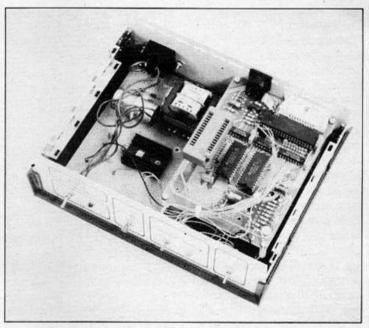

Inside view of a prototype of the BASIC computer.

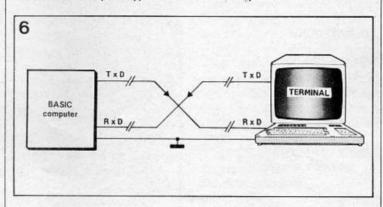


Fig. 6 The 3-wire connection between the BASIC computer and the terminal.

11059200 16 244 52

The system prompt > is displayed to indicate that the computer is ready to accept commands, which are not executed until <CR> is received. Actually, the 8052AH-BASIC starts tokenizing and storing the BASIC commands after receiving a carriage return (ODH). Depending on the length of the line, and the complexity of the command(s), this takes some time, and new characters must not be sent until the CPU responds with the prompt, indicating completion of the storage process.

The BASIC computer is probably best programmed and controlled with the aid of a personal micro sporting an RS232 port. As to software, a terminal emulation or communication program in conjunction with a wordprocessor enables efficient editing and downloading of BASIC files. A general flowchart of a serial I/O routine to support the above

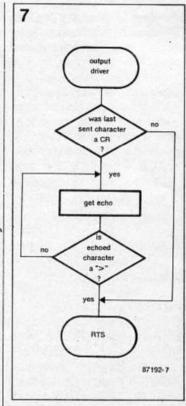


Fig. 7 The sending computer must wait for the > prompt from the BASIC computer before sending a new line of commands.